## KNOWLEDGE ORGANISER :: LOGIC


### KEY VOCABULARY

Logic	A system designed to perform a task according to string principles and rules			
Logic Gate	The physical switches inside an electronic device which are able to perform calculations			
Logic Circuit	A series of logic gates combined to perform a specific task			
Truth Table	A table used to plan the inputs and outputs from a logic circuit			
Boolean	True or False			
Operator	A mathematical symbol used in computing			
+	Addition			
-	Subtraction			
1	Division			
*	Multiplication			
**	Exponent (Power Of)			
MOD	Modulus Division Divide one number by another and return the remainder			
DIV	Integer Division Divide one number by another and return the whole number value			

### TRUTH TABLES


**Truth Tables** are used to plan the different inputs for a logic gate or logic circuit and show the different outputs

# (NOTA) OR (BANDC)

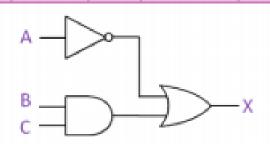
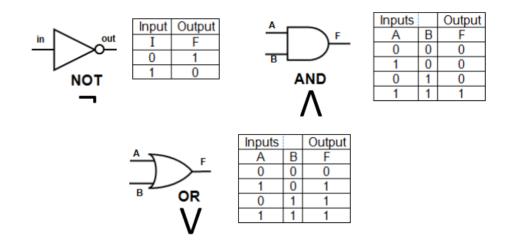
### LOGIC GATES

Logic Gates take an input (labelled A, B or C) and provide a single output



### LOGIC CIRCUITS

A **Logic Circuit** is a combination of different logic gates Logic gates can be combined in any order to solve computational problems In the CPU, the transistors are the logic gates

A	В	С	NOT A	B AND C	X = (NOT A) OR (B AND C)
0	0	0	1	0	1
0	0	1	1	0	1
0	1	0	1	0	1
0	1	1	1	1	1
1	0	0	0	0	0
1	0	1	0	0	0
1	1	0	0	0	0
1	1	1	0	1	1